KIET GROUP OF INSTITUTIONS · ASSIGNMENT QUESTION 4

EMERGENCY PANIC ALARM PCB DESIGN

Design and Development Using KiCad

Student Name: Shaurya Upadhyay

Department: Electrical and Electronics Engineering (EEE)

Institution: KIET Group of Institutions

Subject: PCB Design

Assignment: Question 4

Made with GAMMA

INTRODUCTION

An Emergency Panic Alarm System

An Emergency Panic Alarm System is an electronic safety device designed to alert nearby people during an emergency.

- It uses a push button to activate the alarm.
- A buzzer produces an audible warning.
- A red LED provides a visual indication.
- The circuit operates using a 5V DC power supply.
- The system provides a simple and quick emergency alert.

Objective: To design a simple, low-cost and reliable emergency alarm PCB using KiCad.

Made with GAMMA

PROBLEM STATEMENT

Delayed help in emergencies

In offices and workplaces, employees may need immediate assistance during unexpected emergencies.

Traditional methods of requesting help may cause delays.

Proposed Solution:

- Install a panic button at an accessible location.
- Pressing the button activates the buzzer.
- The warning LED turns ON simultaneously.
- Nearby personnel can identify the emergency and respond quickly.

Made with GAMMA

COMPONENTS REQUIRED

Components Required

Component	Specification	Quantity
Push Button	Normally Open Tactile Switch	1
Buzzer	5V Active Buzzer	1
LED	Red LED, 5mm	1
Resistor	330Ω, ¼W	1
Capacitor C1	100µF, 16V	1
Capacitor C2	10µF, 16V	1
Connector	2-Pin Terminal Block	1

Made with GAMMA

WORKING PRINCIPLE

Working Principle

1. The circuit receives a regulated 5V DC supply.
2. Initially, the push button remains open.
3. When an employee presses the push button, the circuit is activated.
4. Current flows through the LED and buzzer branches.
5. The LED glows and the buzzer produces an audible alarm.
6. When the button is released, the alarm stops.


Result: Both visual and audible alerts are generated simultaneously.

Made with GAMMA

CIRCUIT SCHEMATIC

Circuit Schematic

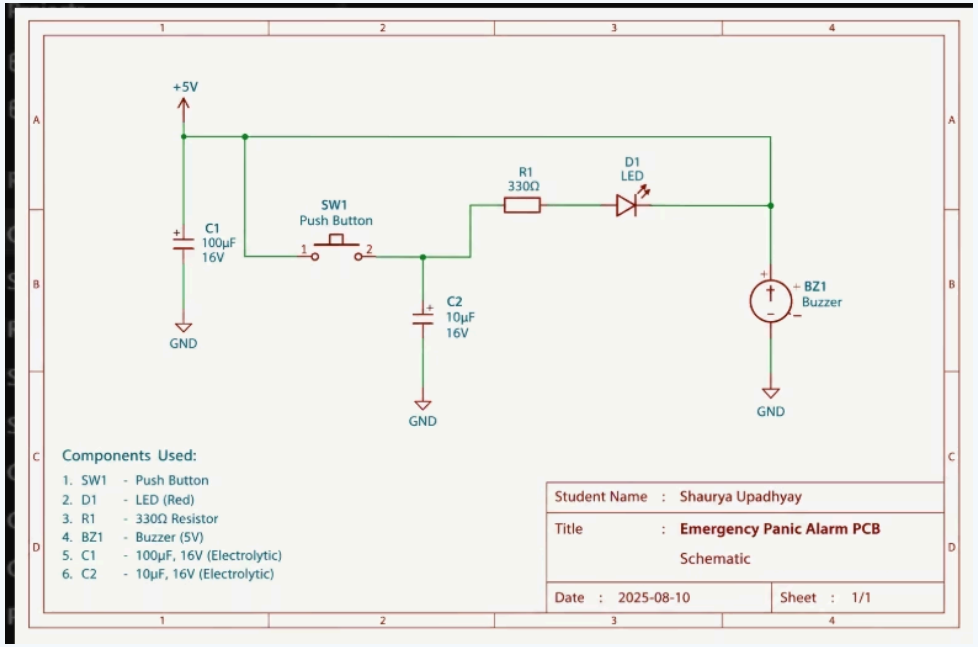The circuit schematic represents the electrical connections between all electronic components.



MAIN COMPONENTS AND THEIR FUNCTIONS

- **SW1:** Acts as the emergency activation switch.
- **R1:** Limits the current flowing through the LED.
- **D1:** Provides a visual warning indication.
- **BZ1:** Produces an audible warning.
- **C1:** 100µF capacitor for supply filtering.
- **C2:** 10µF capacitor for additional filtering.
- **J1:** Provides the 5V DC power input.


Software Used: KiCad Schematic

Made with GAMMA

FOOTPRINT ASSIGNMENT

Footprint Assignment

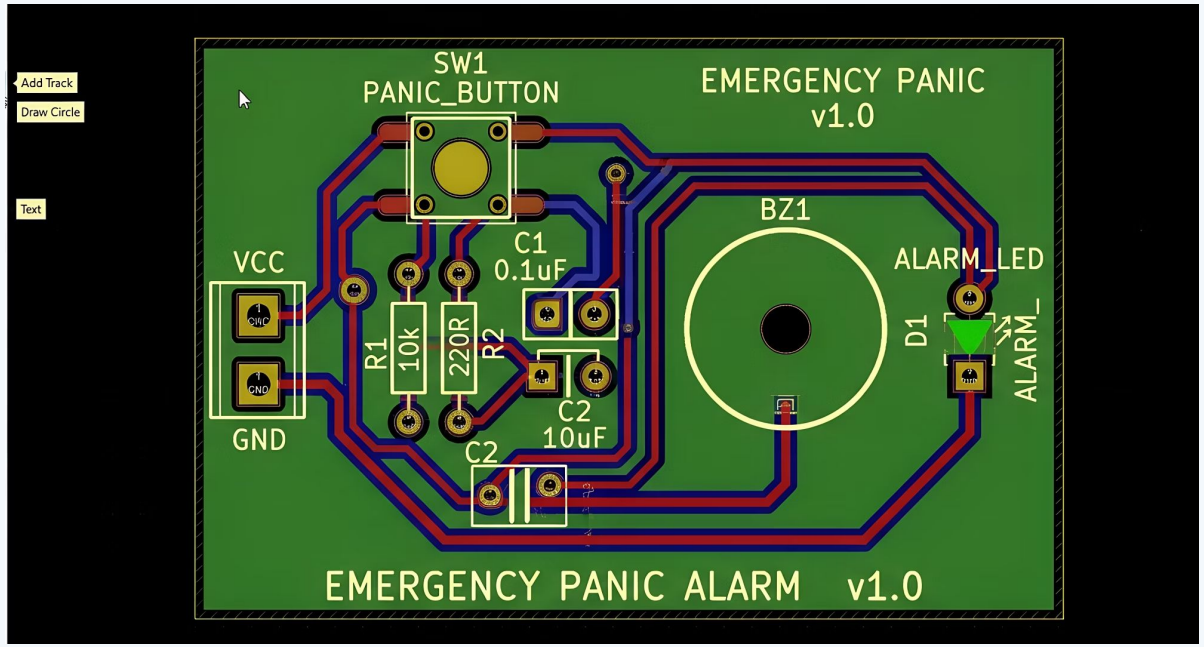A footprint represents the physical dimensions and pad arrangement of an electronic component on a PCB.



Component	Suggested Footprint
SW1	SW_PUSH_6mm
BZ1	Buzzer_12x9.5mm
D1	LED_D5.0mm
R1	R_Axial_DIN0207
C1	CP_Radial_D6.3mm
C2	CP_Radial_D5.0mm
J1	TerminalBlock_2P_5.00mm


Importance of Footprint Assignment:

- Ensures correct component placement.
- Matches PCB pads with physical component leads.
- Helps avoid manufacturing errors.
- Improves assembly accuracy.

Made with GAMMA

PCB Layout and Routing

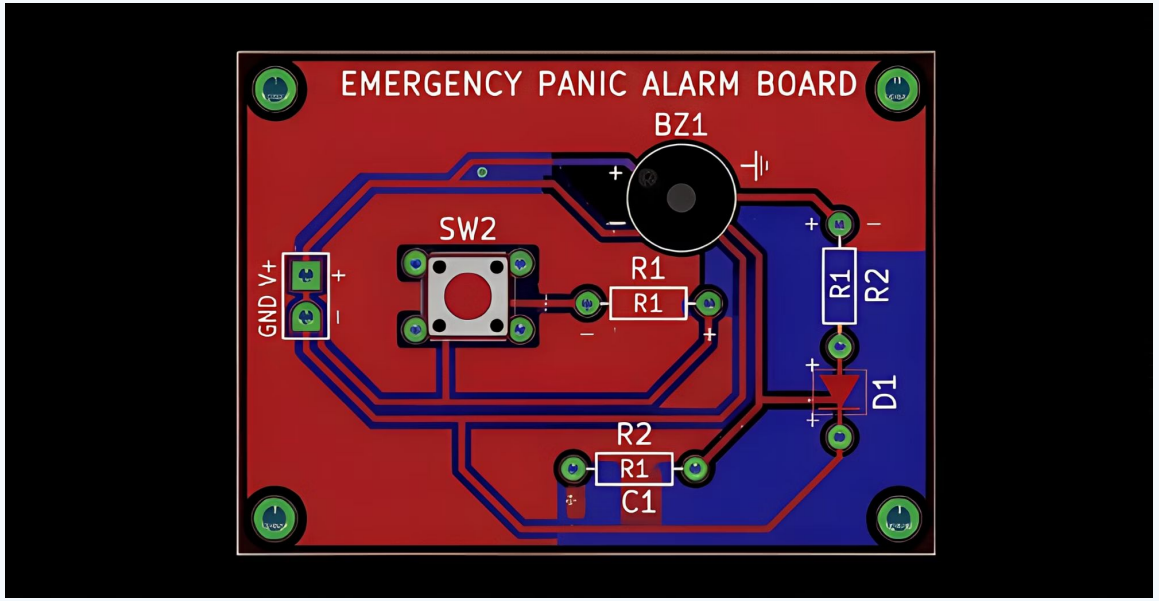PCB layout involves arranging electronic components and connecting them using copper tracks.



DESIGN CONSIDERATIONS

- Place components according to circuit requirements.
- Keep connections short and organized.
- Maintain sufficient spacing between tracks.
- Use suitable track widths.
- Provide mounting holes where required.
- Verify electrical connections using the Design Rules Checker (DRC).

Software Used: KiCad PCB Editor


Made with GAMMA

2D and 3D PCB Views

2D PCB View

The 2D view displays the component footprints, pads, copper tracks and board boundaries.

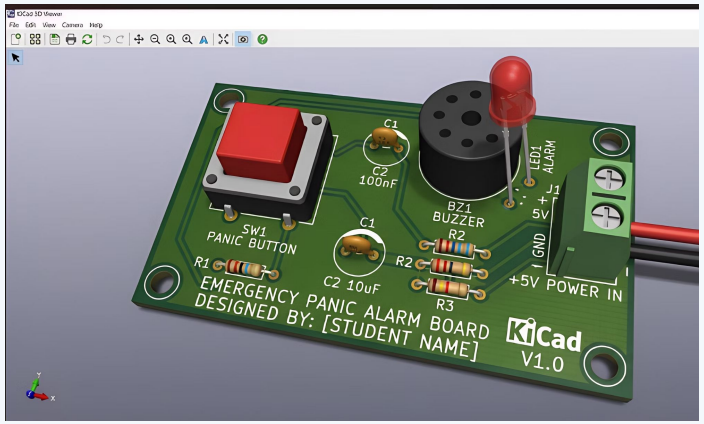It helps in checking the component arrangement and routing connections.



3D PCB View

The 3D viewer provides a realistic visualization of the PCB with mounted components.

It helps in understanding the physical appearance and placement of components before manufacturing.

Made with GAMMA

Bill of Materials (BOM)

The Bill of Materials provides a complete list of components required to assemble the PCB.

S.No.	Component	Reference	Quantity
1	Push Button	SW1	1
2	Buzzer	BZ1	1
3	Red LED	D1	1
4	330Ω Resistor	R1	1
5	100µF Capacitor	C1	1
6	10µF Capacitor	C2	1
7	2-Pin Connector	J1	1

Total Components: 7



Made with GAMMA

Gerber File Generation

Gerber files are standard manufacturing files used to fabricate printed circuit boards.

Steps for Generating Gerber Files:

1. Open the PCB Editor in KiCad.
2. Check the PCB layout and routing.
3. Open the Plot option.
4. Select the required copper and fabrication layers.
5. Generate the Gerber files.
6. Generate the drill files separately.
7. Save all manufacturing files in a dedicated folder.

Made with GAMMA

CONCLUSION

Conclusion

The Emergency Panic Alarm PCB demonstrates the practical application of basic electronic components and PCB designing.

- A push button provides emergency activation.
- The buzzer generates an audible alert.
- The LED provides a visual warning.
- KiCad helps in schematic creation, footprint assignment and PCB layout.
- The design can be used as a basic emergency alert system.

Future Improvements:

- Add a wireless notification system.
- Include a battery backup.
- Add a latching mechanism to keep the alarm active until reset.
- Add multiple panic buttons for different office locations.

Made with GAMMA

THANK YOU

Emergency Panic Alarm PCB Design Using KiCad

Submitted by: Shaurya Upadhyay

Department of Electrical and Electronics Engineering

KIET Group of Institutions

Made with GAMMA